

Combinational Logic



Chapter 4

- Agenda
- Combinational Logic
 - Design Procedure
 - Adders, Subtractors
 - Analysis Procedure
 - Multilevel Logic Circuit
- Reading
- Mano: Ch 4
- Project #1

- Objectives:
 - Understand the nature of Combinational Logic
 - Understand and able to execute the combinational logic
 - design procedure

Combinational Logic : Definition

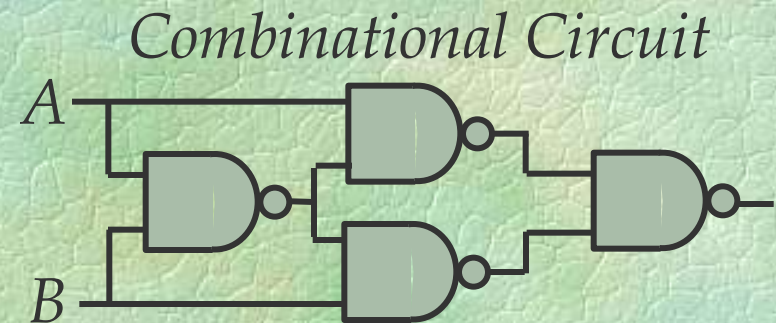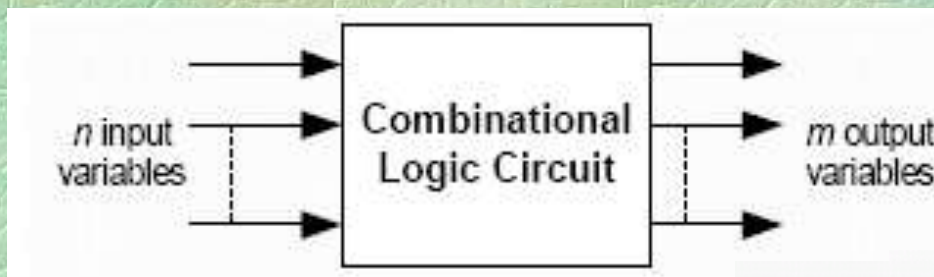- Combinational Logic is a logical circuit consists of logic gates whose outputs at any time are determined directly from the present combination of inputs without regard to previous inputs



Analysis Procedure:

$$F_2 = AB + AC + BC$$

$$T_1 = A + B + C$$

$$T_2 = ABC$$

and

$$T_3 = F_2' T_1$$

$$F_1 = T_3 + T_2$$

Therefore,

$$F_1 = T_3 + T_2 = F_2' T_1 + ABC$$


$$= (AB + AC + BC)'(A + B + C)$$

$$+ ABC$$

$$= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC$$

=

$$= A'BC' + A'B'C + AB'C' + ABC$$

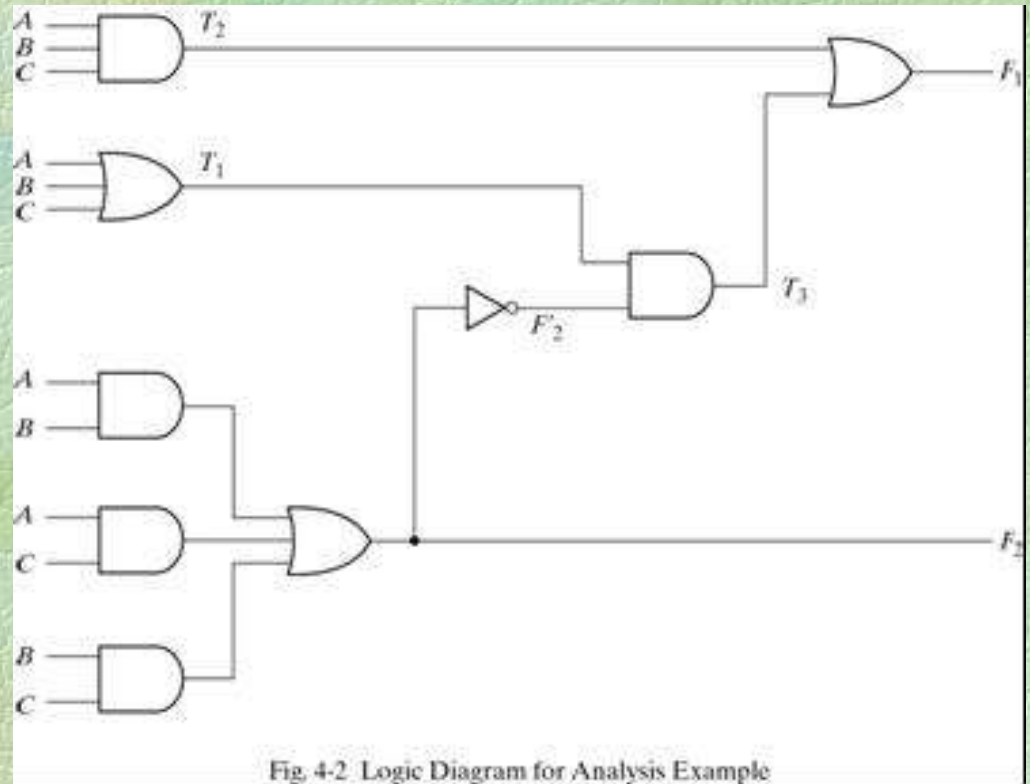

Design Procedure:

- 1. Define the problem**
- 2. Define the input/output variables**
- 3. Truth table of the relationships**
- 4. Simplify Boolean functions**
- 5. Draw the logic diagram**

Constraints:

1. Min No. of gates
2. Minimum number of inputs to a gate
3. Min Propagation time
4. Min no. of interconnections

Example: Code Conversion (BCD to Excess-3)

<i>Input BCD</i>					<i>Output Excess-3</i>			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>		<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0		0	0	1	1
0	0	0	1		0	1	0	0
0	0	1	0		0	1	0	1
0	0	1	1		0	1	1	0
0	1	0	0		0	1	1	1
0	1	0	1		1	0	0	0
0	1	1	0		1	0	0	1
0	1	1	1		1	0	1	0
1	0	0	0		1	0	1	1
1	0	0	1		1	1	0	0


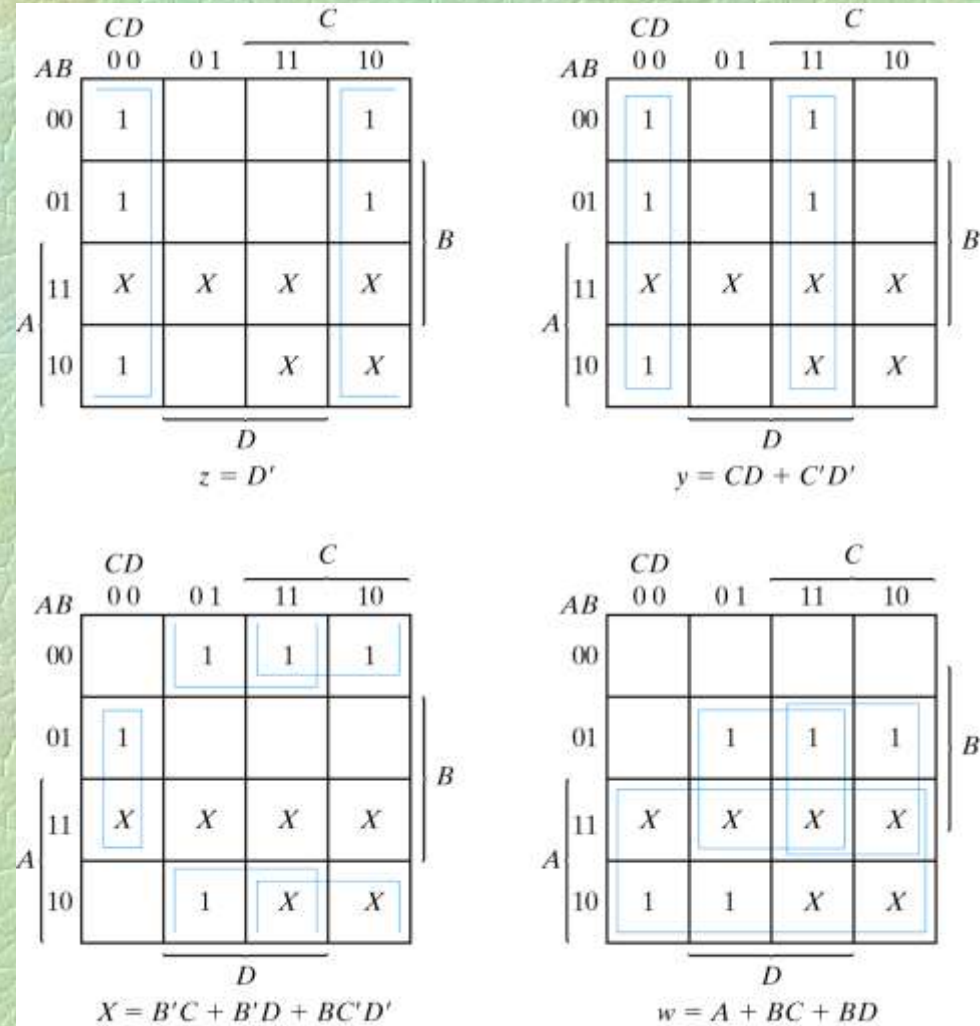


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

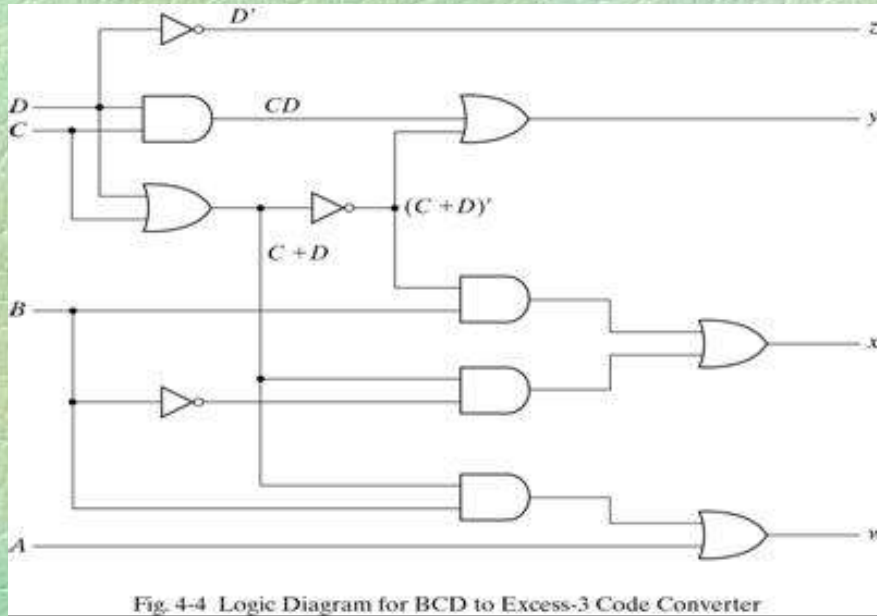Example: Code Conversion (BCD to Excess-3)




$$Z = D'$$

$$y = CD + C'D' = CD + (C+D)'$$

$$\begin{aligned} X &= B'C + B'D + BC'D' = B'(C+D) + BC'D' \\ &= B'(C+D) + B(C+D)' \end{aligned}$$

$$W = A + BC + BD = A + B(C+D)$$

 

Common Combinational Logic

Binary Adders

- Half-Adders
- Full-Adders

Binary Subtractors

- Half-Subtractors
- Full-Subtractors
- Decoders/Encoders
- Multiplexers

Binary Adders

- One of the basic arithmetic process in computer system
- One that performs the addition of 2 bits is Half-Adder
- One that performs the addition in 3 bits (2 significant bits and a previous carry) is called Full-Adder

Half-Adder

2 Input & 2 output

- The truth table
- Thus the Boolean Function is
- $S = x'y + xy'$;
- $C = xy$
- The function cannot be further simplified

Truth Table

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half-Adder Implementations

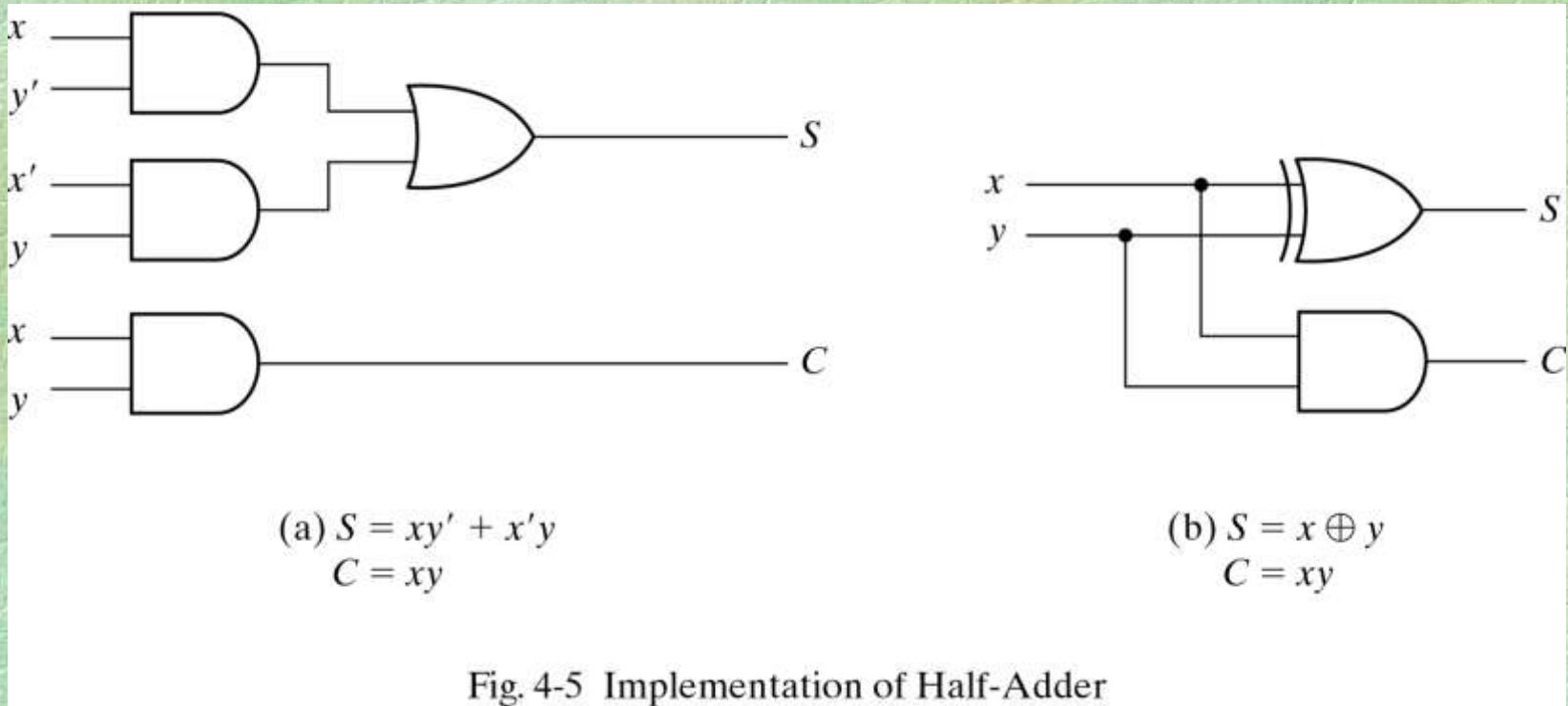



Fig. 4-5 Implementation of Half-Adder

Full-Adder Truth Table


- 3 Input (x & y as the input and z as the previous carry), & 2 output (s, c)
- The truth table is :

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full-Adder Map

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$C = xy + xz + yz$$

$$= xy + xy'z + x'yz$$

Fig. 4-6 Maps for Full Adder

Full-Adder Simple Implementation

- Logic Expression

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

- Implementation

 


Fig. 4-7 Implementation of Full Adder in Sum of Products

Full-Adder Implementation

$$\begin{aligned} S &= z \oplus (x \oplus y) \\ &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= xy'z' + x'yz' + xyz + x'y'z \end{aligned}$$

$$\begin{aligned} C &= z(xy' + x'y) + xy \\ &= xy'z + x'yz + xy \end{aligned}$$


 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

Full-Adder Application

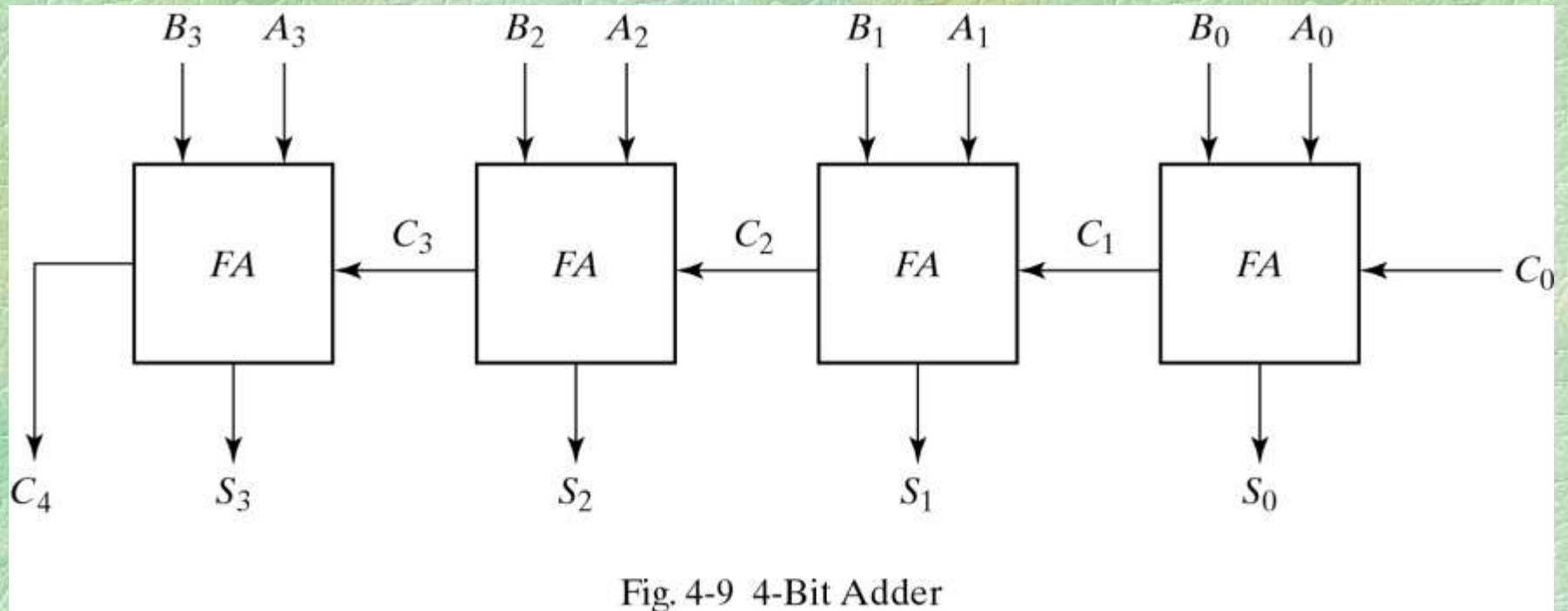

Example:

A=1011, B=0011 then S= 1110

Subscript i	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Full-Adder Other Implementation

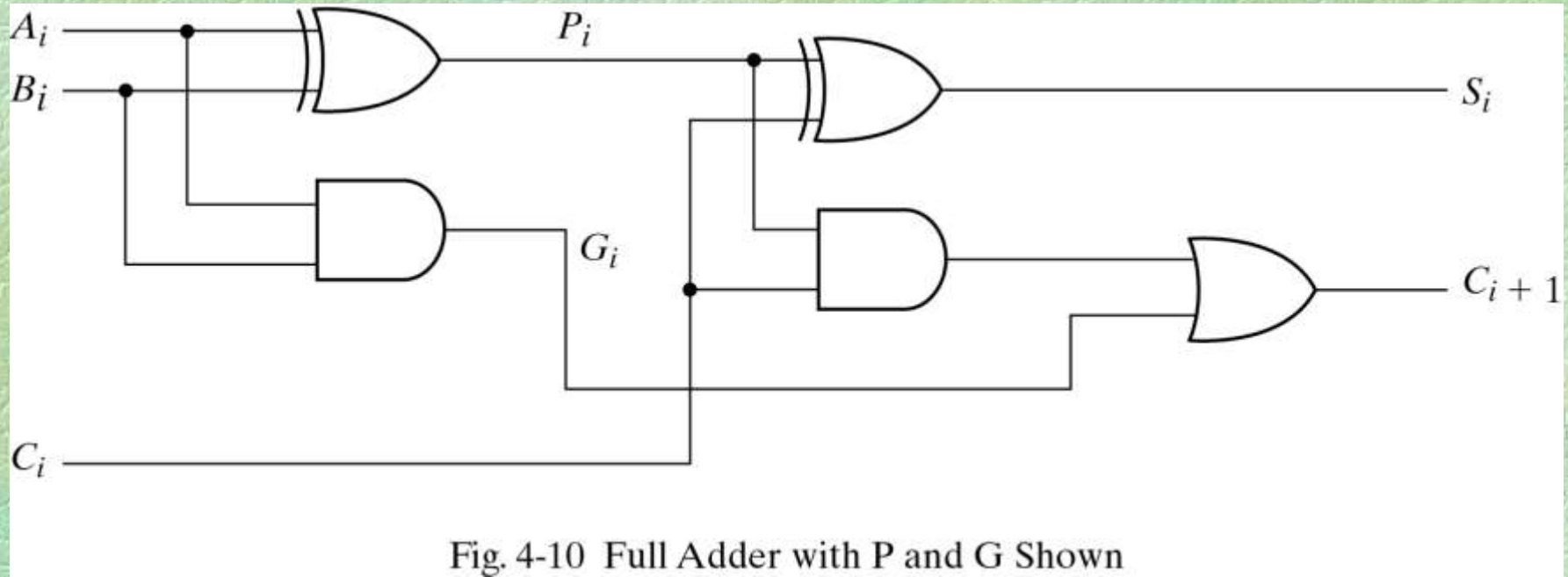


Fig. 4-10 Full Adder with P and G Shown

$$P_i = A_i \oplus B_i$$
$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$
$$C_{i+1} = G_i + P_i C_i$$

G_i : Carry generate
 P_i : Carry propagate

Carry Propagation:

- *The total propagation time is equal to the propagation delay of a typical gate times the number of gate levels in the circuit.*

C_0 =input carry

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

Carry lookahead Generator

C_0 = input carry

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

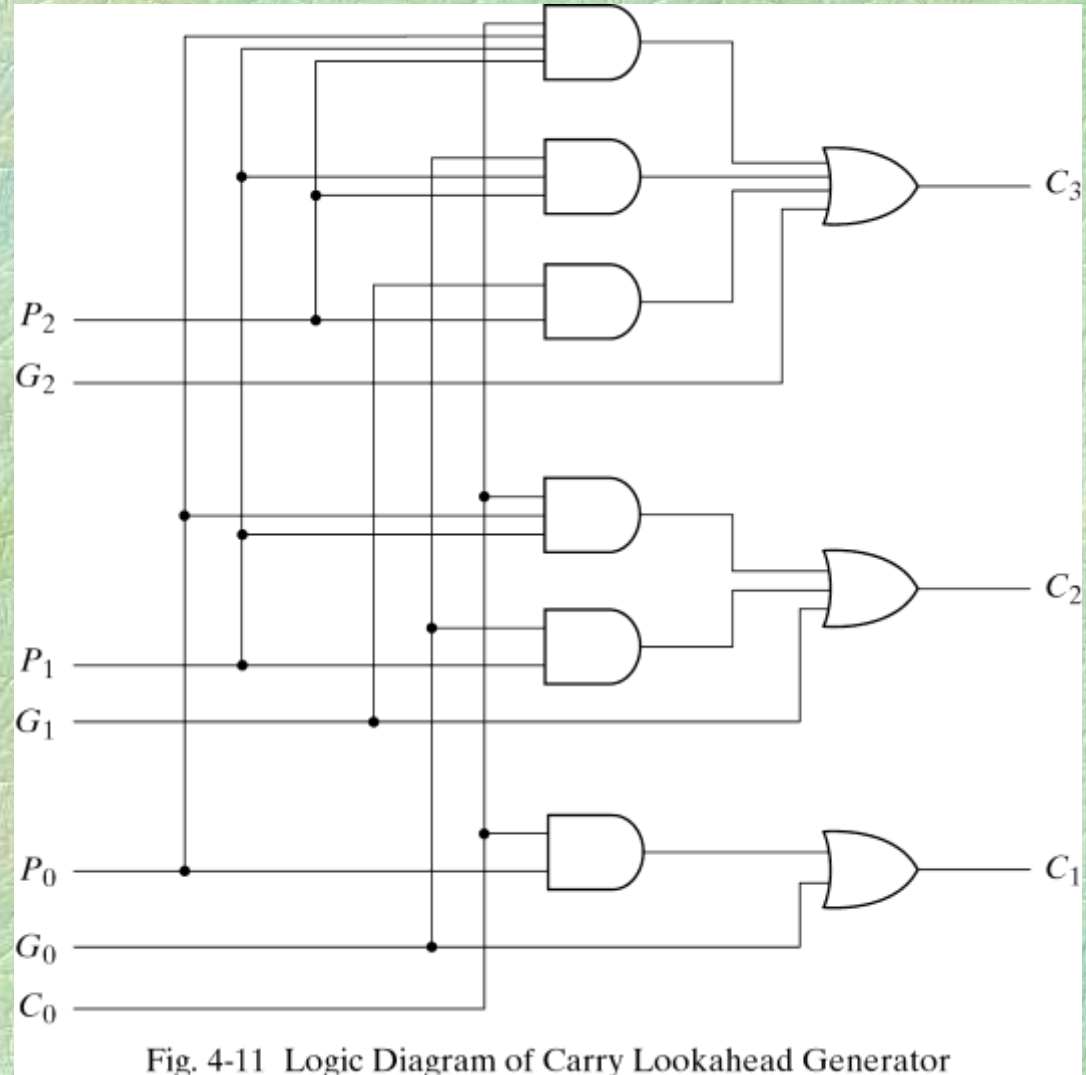


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

Adder with carry lookahead Generator

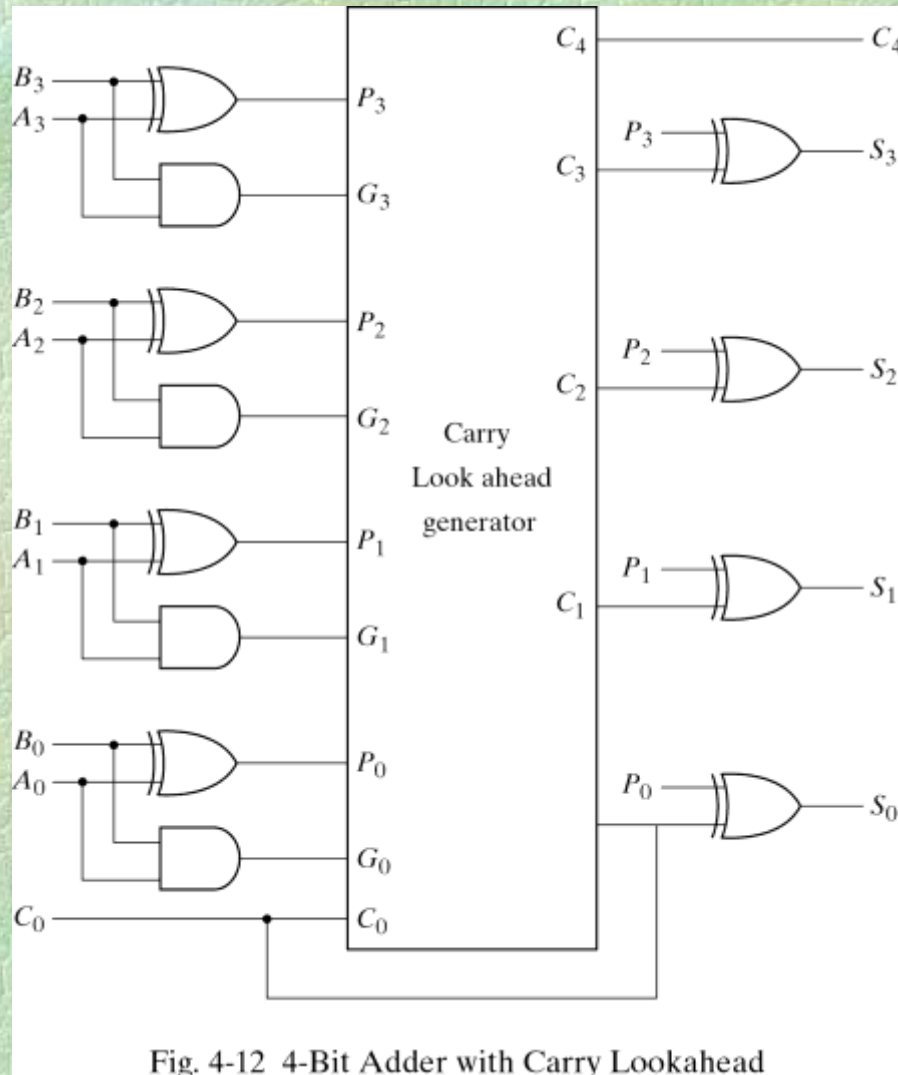


Fig. 4-12 4-Bit Adder with Carry Lookahead

Binary Subtractors

- One of the basic arithmetic process in computer system
- One that subtracts 2 and produce their difference is Half-Subtractor
- One that subtracts 2 and produce their difference while taking account that 1 have been borrowed by a lower significant stage.
- it is called : Full-Subtractor

Half-Subtractor

- 2 Input & 2 output (Borrow & Data)
- Boolean Function cannot be simplified
- $D = x'y + xy'$
- $B = x'y$

Truth table

X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

Full-Subtractor

- You do it
- Truth table
- Simplify with K-Map
- Draw the Logic Gate

D	00	01	11	10
0		1		1
1	1		1	

B	00	01	11	10
0		1	1	1
1			1	

x	y	z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$D = x'y'z + x'yz' + xy'z' + xyz$$

$$B = x'y + x'z + yz$$

Adder-Subtractor

- The operation $A-B = A + \text{“1’s complement of B”} + 1$
 $= A + \text{“2’s complement of B.”}$
- For unsigned numbers, this gives $A-B$ if $A \geq B$ or the 2’s complement of $(B-A)$ if $A < B$.
- For signed numbers the result is $A-B$ provided that there is no overflow.
- The addition and subtraction operations can be combined into one circuit with one common binary adder and including an X-OR gate with each full adder.

Adder-Subtractor

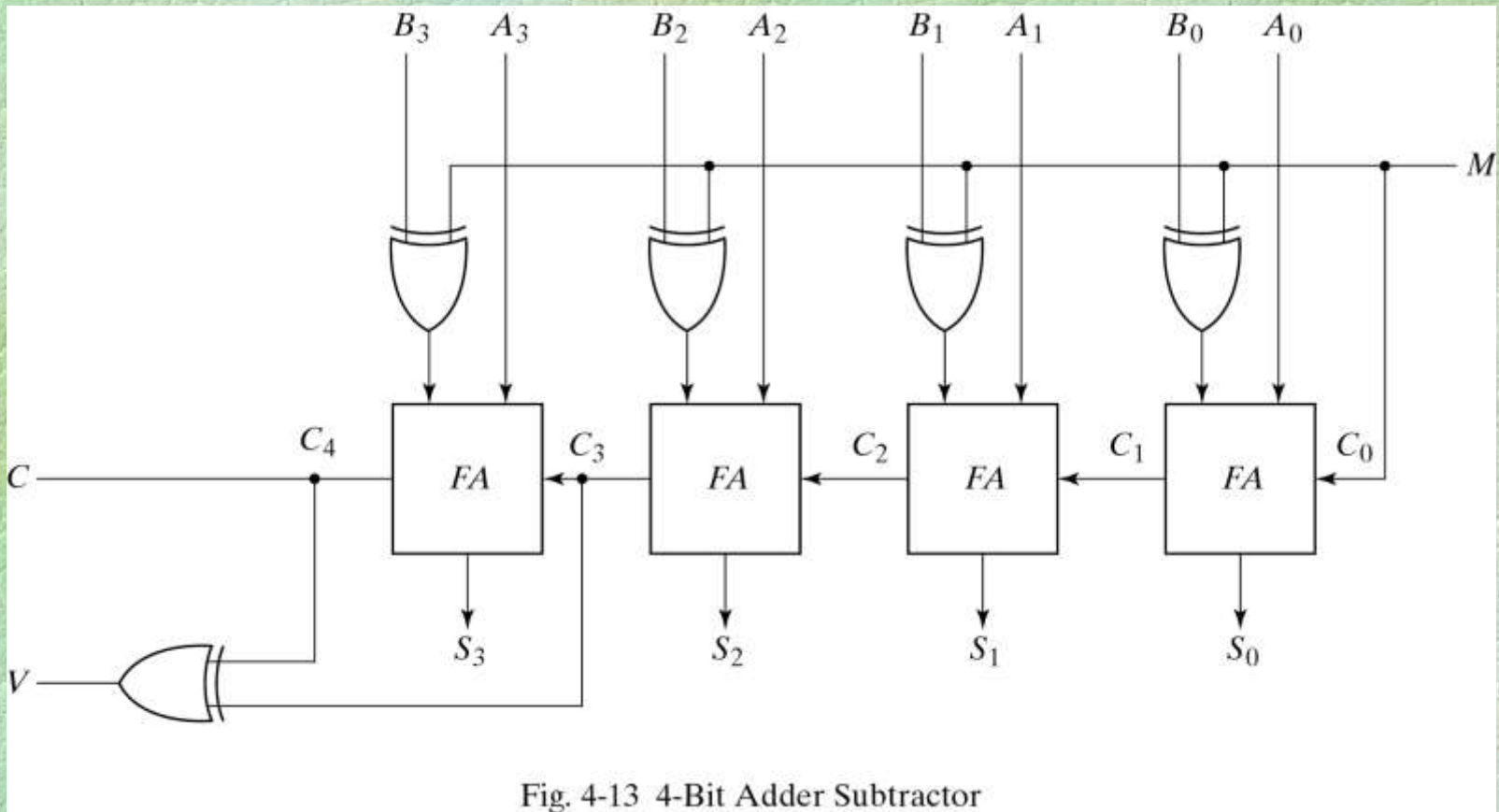

When $M=0$, the circuit is adder (since $B \oplus 0 = B$), and when $M=1$, the circuit is subtractor (since $B \oplus 1 = B'$).

Overflow

Carries: 0 1

+70	0	1000110
+80	0	1010000
<hr/>		
+150	1	0010110

carries: 1 0

-70	1	0111010
-80	1	0110000
<hr/>		
-150	0	1101010

Binary Multiplier

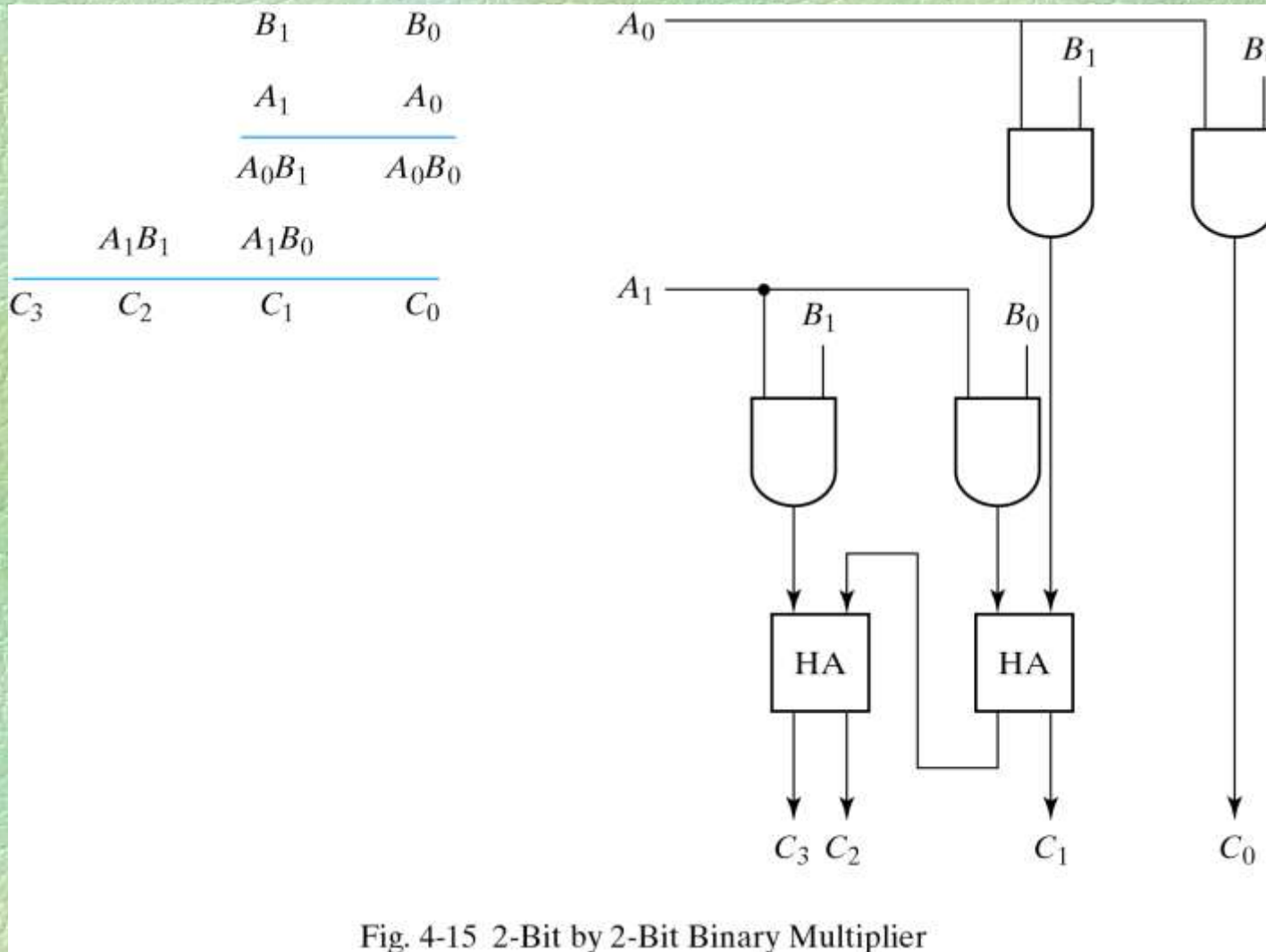


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

4 by 3 Binary Multiplier


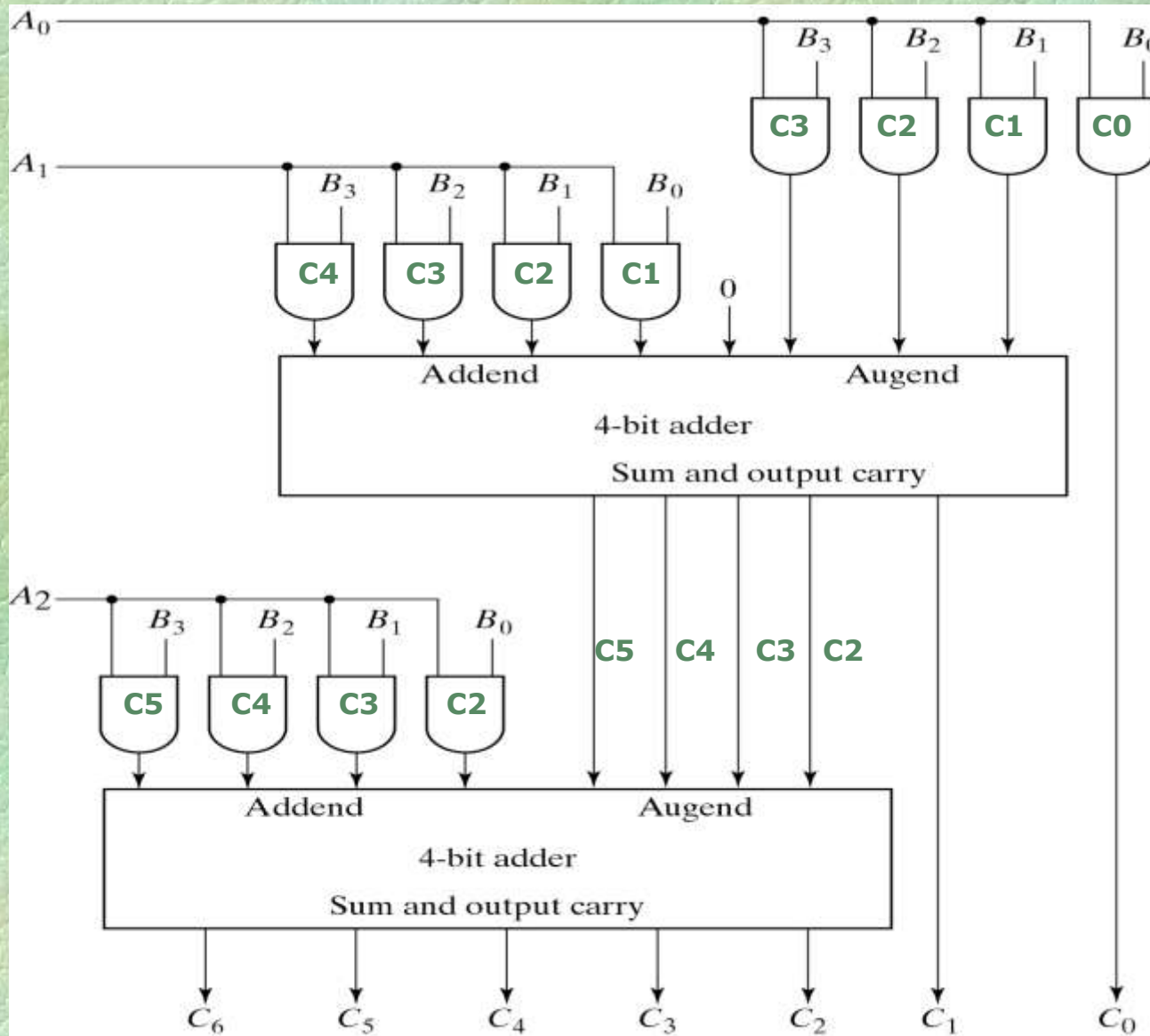


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

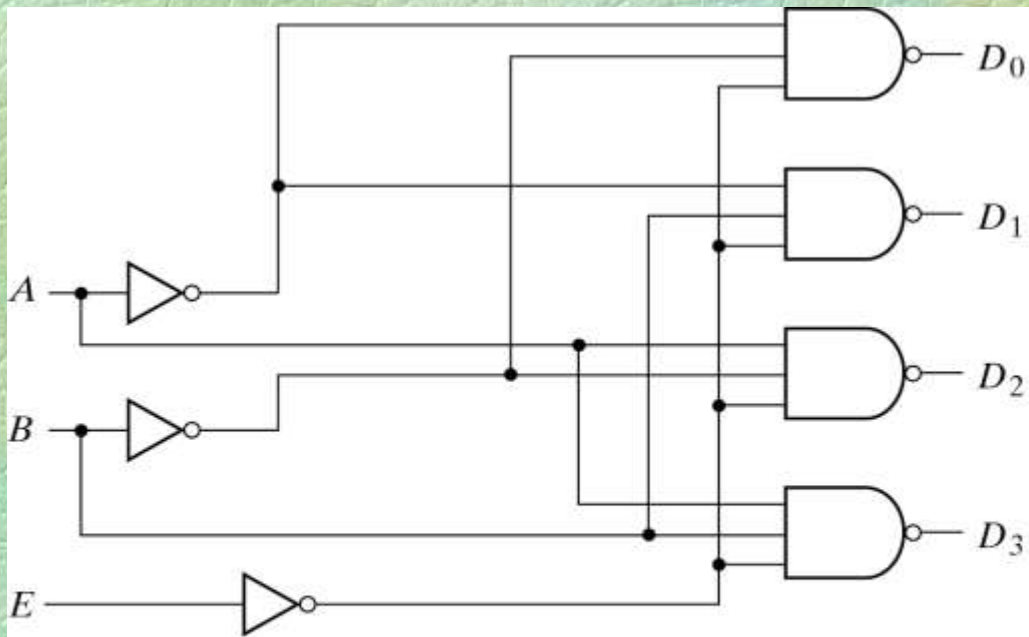2-4 Line Decoder (1-4 line Demultiplexer)



(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input